

CPU DESIGN LAB REPORT

CS2310 VERILOG LAB 4

Name : G ASISH SAI

Roll No : CS21B031


Batch No : 11

All modules are explained in detail along with the test bench and relevant waveform snapshots/outputs below.

CPU_tb.v

- The instruction is separated into operation code, operand 1, operand2 and given as inputs to module **CU(control unit)**.
- The output is stored in result.

```
1  `timescale 1ns/1ps
2
3  module CPU_tb();
4
5      reg [18:0] instruction;
6      wire [7:0] result;
7
8      //Providing Operation code and operands seperately to the control unit(cu).
9      CU uut(result, instruction[18:16], instruction[15:8], instruction[7:0]);
10
11  initial begin
12
13      $dumpfile ("CPU_tb.vcd");
14      $dumpvars (0,CPU_tb);
15
16
17      instruction = 19'b0010010001100010100; #20; //Addition
18      instruction = 19'b0100010001100010100; #20; //Subtraction
19      instruction = 19'b0110010001100010100; #20; //Bitwise And
20      instruction = 19'b1000010001100010100; #20; //Bitwise or
21      instruction = 19'b1010010001100010100; #20; //Bitwise Not
22      instruction = 19'b1100010001100010100; #20; //Increment
23      instruction = 19'b1110010001100010100; #20; //Decrement
24
25      $display("Test Completed");
26
27  end
28
29 endmodule
```

 

CU.v

- In this module op indicates operation code, operand1 and operand2 are the operands.
- Operand1 and Operand2 are sent as inputs to **ALU(Arithmetic and logic unit)**. The 7 outputs(x1 to x7) returned are the respective results in the 7 operations. (Operations are taken in the order given with addition being given index 1)
- Now the idea of Decoder is used to find which operation the operation code corresponds to. opcode[i] in the module is 1 if it represents the ith operation. (Operations are numbered in the same way as the outputs)
- Now the idea of Multiplexer is used to copy the output of the corresponding operation into the result.

(1) An AND operation is implemented on each output (xi) and its opcode (opcode[i]) and stored in temporary variables (temp1 to temp7) each of 8 bits.

(2) An OR operation is implemented on each of the 8 bits in the 7 temporary variables and the value is stored in the result. The result is returned to the **CPU_tb**.

ALU.v

- In this module operand1 and operand2 are received as inputs.
- Each of the 7 operations are computed as follows.
 - (1) To compute **ADDITION** , operand1 and operand2 are passed as inputs to **fulladder_tb** and output is stored in x1.
 - (2) To compute **SUBTRACTION** , operand1 and 2's complement of operand2 are passed as input to **fulladder_tb** and output is stored in x2.

2's complement of operand2 is computed by applying a NOT over each bit of operand2 and adding 1 by using a full adder (**fulladder_tb**).
 - (3) To compute **INCREMENT** , operand 1 and the literal 8'b00000001 as operand 2 are given as inputs to **fulladder_tb** and output is stored in x3.
 - (4) To compute **DECREMENT** , operand 1 and the literal 8'b11111111 as operand 2 are given as inputs to **fulladder_tb** and output is stored in x4.
 - (5) To compute **AND** , operand 1 and operand 2 are given as inputs to **and12** and output is stored in x5.
 - (6) To compute **OR** , operand 1 and operand 2 are given as inputs to **or12** and output is stored in x6.
 - (7) To compute **NOT** , operand 1 is given as input to **not1** and output is stored in x7.
- The 7 outputs (x1 to x7) are returned to **CU**.

Time	
operand1[7:0] =00100011	00100011
operand2[7:0] =00010100	00010100
x1[7:0] =00110111	00110111
x2[7:0] =00001111	00001111
x3[7:0] =00100100	00100100
x4[7:0] =00100010	00100010
x5[7:0] =00000000	00000000
x6[7:0] =00110111	00110111
x7[7:0] =11011100	11011100

The outputs (x1 to x7) of the 7 given operations for two operands given in the test bench.

fulladder_tb.v

- This module is called multiple times in **ALU**, operand1 and operand2 Each consisting of 8 bits are given as inputs.
- An [8:0] carry array is declared as well to store the carry. carry[0] is initialized to 0 using an AND gate.
- - (1) **fulladder** module is called 8 times, each time passing ith bit of operand1, operand2, carry as input.
 - (2) A carry is returned which is stored in (i+1)th bit of carry array, and a sum is returned which is stored in the ith bit of sum array.
- The sum array is returned to the **ALU**.

fulladder.v

- In this module a, b, carry_in are received as inputs.
- To implement a full adder, I am implementing two half adders. Half adder is implemented by using an XOR and an AND gate.
- The inputs of the first half adder are a,b and outputs are stored in temp1 and temp2 (temporary variables).
- The inputs of the second half adder are temp1 and carry_in and outputs are stored in sum and temp3. An OR gate is implemented over temp2 and temp3 to obtain carry_out.
- carry_out and sum are returned as outputs to **fulladder_tb**.

Time	100 ns				
operand1[7:0]	00100011	11100011	00100010	00101111	00100011
operand2[7:0]	00010100	00010110	00110100	00011100	00010100
carry[8:0]	00000000	00000100	00100000	00111100	00000000
sum[7:0]	00110111	11111001	01010110	01001011	00110111

fulladder_tb.v output for 5 different examples(not the test bench one)

and12.v

- In this module operand1, operand2 are given as inputs.
- An AND operation is implemented over 8 bits of operand1, operand2 and the output is stored in and_out.
- and_out is returned as output to **ALU**.

Time	100 ns				
operand1[7:0]	00100011	11100011	00100010	00101111	00100011
operand2[7:0]	00010100	00010110	00110100	00011100	00010100
and_out[7:0]	00000000	00000010	00100000	00001100	00000000

and12.v output for 5 different examples (not the test bench one)

or12.v

- In this module operand1, operand2 are given as inputs.
- An OR operation is implemented over 8 bits of operand1, operand2 and the output is stored in or_out.
- or_out is returned as output to **ALU**.

Time	0	1	2	3	4	5	6	7	8
operand1[7:0] = 00100011	00100011	11100011	00100010	00101111	00100011				
operand2[7:0] = 00010100	00010100	00010110	00110100	00011100	00010100				
or_out[7:0] = 00110111	00110111	11110111	00110110	00111111	00110111				

or12.v output for 5 different examples (other than the one in the test bench).

not1.v

- In this module operand1 is given as inputs.
- A NOT operation is implemented over 8 bits of operand1 and the output is stored in not_out.
- not_out is returned as output to **ALU**.

Time	0	1	2	3	4	5	6	7	8
operand1[7:0] = 00100011	00100011	11100011	00100010	00101111	00100011				100
not_out[7:0] = 11011100	11011100	00011100	11011101	11010000	11011100				

not1.v output for 5 different examples (other than the one in the test bench).